


Algoritmos y programación

JUAN PABLO KARAM

Lizbeth Hernández

26/08/2026


PIA7

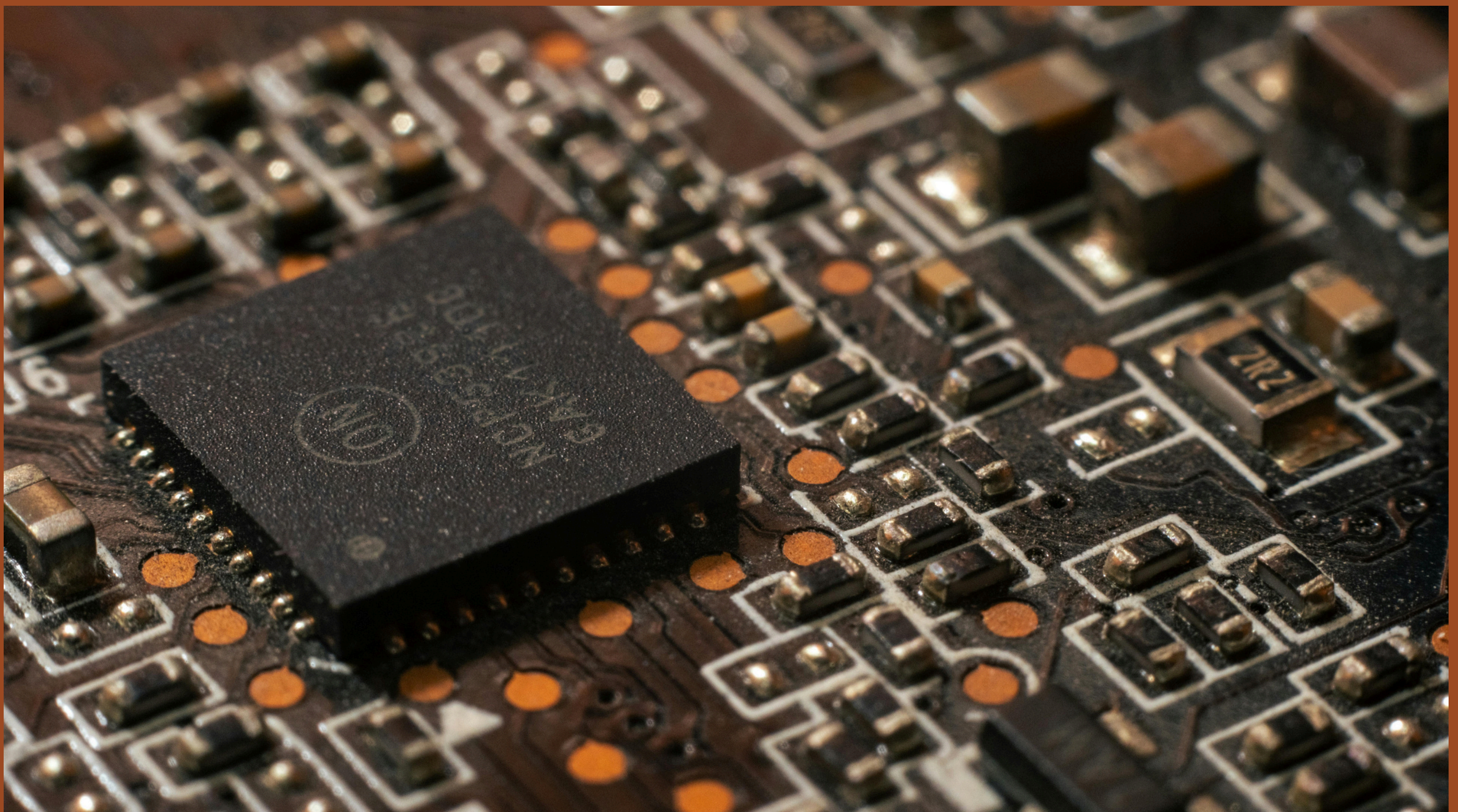

1. (p AND q) OR (NOT p)

Salir de la pantalla completa

p	q	p AND q	NOT q	(p AND q) OR (NOT q)
V	V	V	F	V
V	F	F	V	V
F	V	F	F	F
F	F	F	V	V

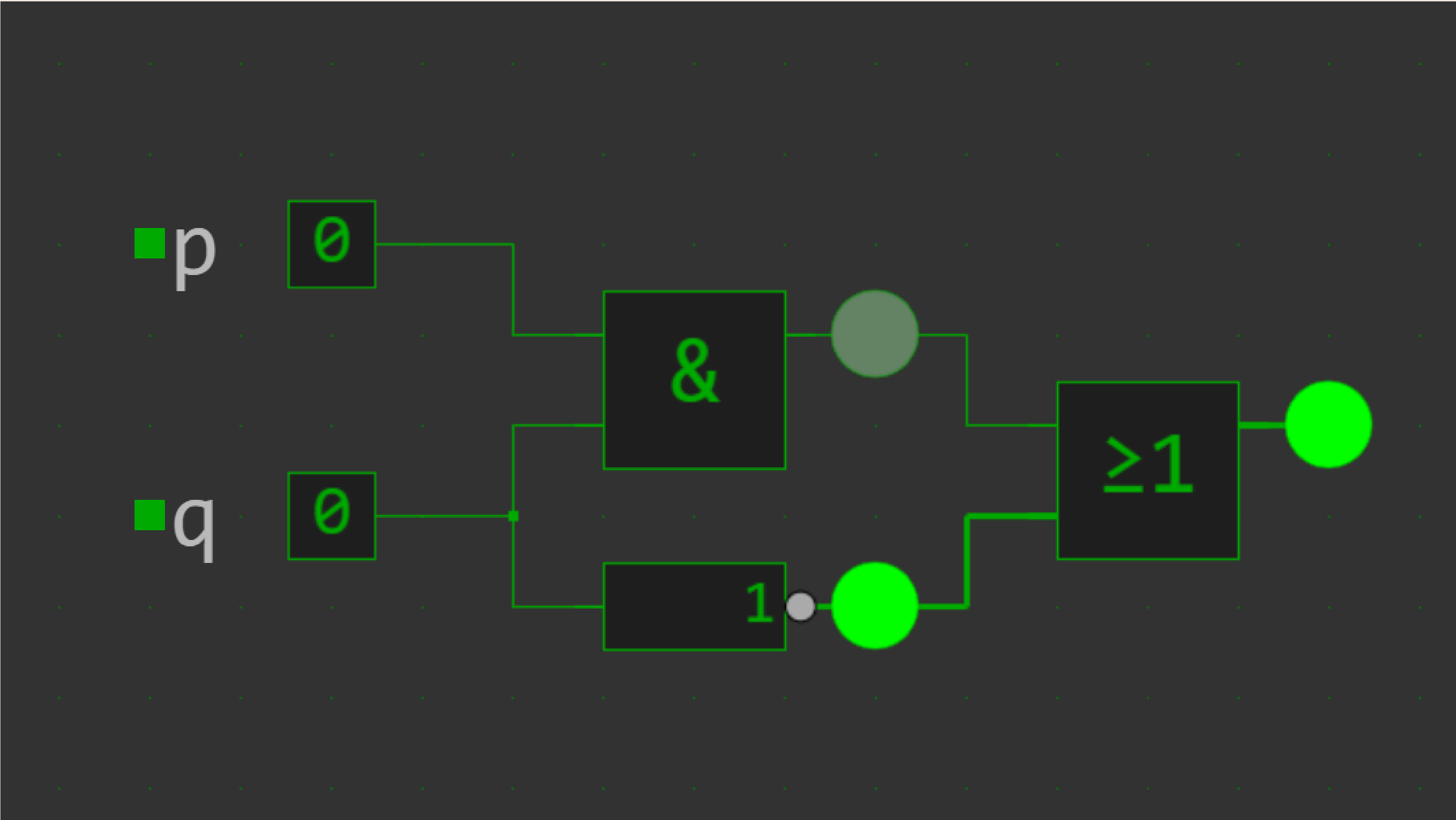

2. NOT (p OR q) AND (p OR q)

Salir de la pantalla completa

p	q	p OR q	NOT (p OR q)	NOT (p OR q) AND (p OR q)
V	V	V	F	F
V	F	V	F	F
F	V	V	F	F
F	F	F	V	F


The diagram illustrates a logic circuit for the expression $\neg(p \vee q) \wedge (p \vee q)$. It features two inputs, p and q , each with a green square indicator and a green box containing the value 0. The circuit consists of the following components and connections:

- An OR gate (labeled ≥ 1) with two inputs connected to the p and q inputs.
- A NOT gate (represented by a green circle) connected to the output of the OR gate.
- A second OR gate (labeled ≥ 1) with one input connected to the output of the first OR gate and another input connected to a green box containing the value 1.
- An AND gate (labeled $\&$) with two inputs: one connected to the output of the second OR gate and the other connected to the output of the first NOT gate.
- The final output of the circuit is represented by a green circle connected to the output of the AND gate.

3. [(p OR q) AND q] OR (NOT q)

Salir de la pantalla completa

p q	p OR q	(p OR q) AND q	NOT q	[(p OR q) AND q] OR (NOT q)
V V	V	V	F	V
V F	V	F	V	V
F V	V	V	F	V
F F	F	F	V	V

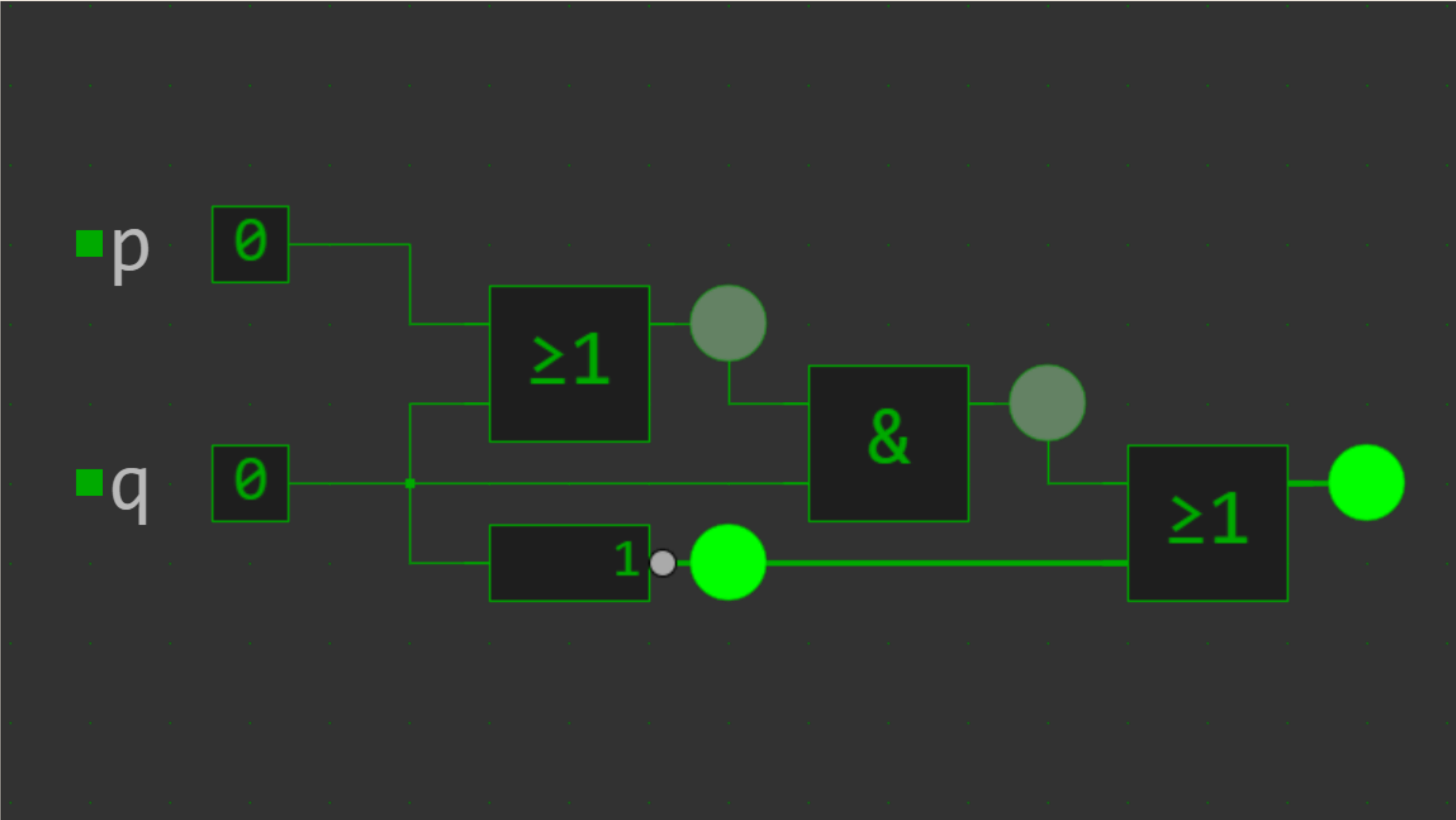

4. [(p OR q) AND q] AND (NOT q)

Salir de la pantalla completa

p q	p OR q	(p OR q) AND q	NOT q	[(p OR q) AND q] AND (NOT q)
V V	V	V	F	F
V F	V	F	V	F
F V	V	V	F	F
F F	F	F	V	F

